

KATHMANDU UNIVERSITY
End Semester Examination [C]
December, 2024

Marks Scored:

Level : B.E.

Year : II

Exam Roll No. :

Time: 30 mins.

Course : EEEG 213

Semester : I

F. M. : 10

Date

19 DEC 2024


Registration No.:

SECTION "A"

[20Q. \times 0.5 = 10 marks]

Choose and encircle in the most appropriate option from each set of choices. Symbols have their usual meaning.


- Time constant of an inductive circuit
 - increases with increase of inductance and decrease of resistance
 - increases with increase of inductance and increase of resistance
 - increases with decrease of inductance and decrease of resistance
 - increases with decrease of inductance and increase of resistance
- The expression of current in R-L circuit is?
 - $i = (V/R)(1 + e^{(R/L)t})$
 - $i = - (V/R)(1 - e^{(R/L)t})$
 - $i = - (V/R)(1 + e^{(R/L)t})$
 - $i = (V/R)(1 - e^{(R/L)t})$
- Which is true for a network that reaches a steady state?
 - Capacitor acts as closed circuit, inductor acts as open circuit
 - Capacitor acts as open circuit, inductor acts as closed circuit
 - Both capacitor and inductor acts as closed circuits
 - Both capacitor and inductor acts as open circuits
- The voltage and current in a capacitor are related as?
 - $I = Cdv/dt$
 - $V = Cdv/dt$
 - $I = Cdv/dt$
 - $V = Cdt/dv$
- Which is true for a network that reaches a steady state?
 - Capacitor acts as closed circuit, inductor acts as open circuit
 - Capacitor acts as open circuit, inductor acts as closed circuit
 - Both capacitor and inductor acts as closed circuits
 - Both capacitor and inductor acts as open circuits
- Which of the following is true for the accompanying figure?
 - $i(0+) = 0, di/dt(0+) = 0, d^2i/dt^2(0+) = K > 0$
 - $i(0+) = 0, di/dt(0+) = K > 0, d^2i/dt^2(0+) = 0$
 - $i(0+) = K > 0, di/dt(0+) = 0, d^2i/dt^2(0+) = 0$
 - $i(0+) = 0, di/dt(0+) = K_1 > 0, d^2i/dt^2(0+) = K_2 < 0$
- The damping coefficient of an parallel RLC circuit is given by
 - $\frac{1}{2}RC$
 - $1/2RC$
 - $R/2L$
 - $1/2R$
- Laplace transform changes the _____ domain function to the _____ domain function.
 - time, time
 - time, frequency
 - frequency, time
 - frequency, frequency

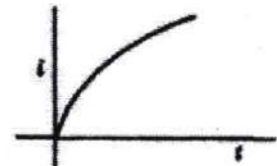

9. The integral of a step function varies linearly with time, which is also known as
- A doublet function
 - A unit doublet function
 - A ramp function
 - An impulse function

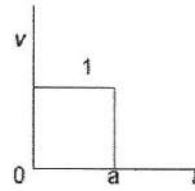
10. The Laplace transform of a pulse shown is given as

- $V(s) = 1/(s-a)$
- $V(s) = (1/s)e^{-as}$
- $V(s) = (1/s)(1-e^{-as})$
- $V(s) = (1/s)(1-e^{as})$



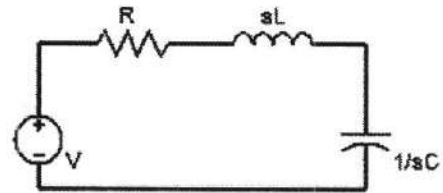
11. In the circuit shown below, if voltage across the capacitor is defined as the output signal of the circuit, then the transfer function is?

- $H(s) = 1/(s^2 LC - RCS + I)$
- $H(s) = 1/(s^2 LC + RCS + I)$
- $H(s) = 1/(s^2 LC + RCS - I)$
- $H(s) = 1/(s^2 LC - RCS - I)$



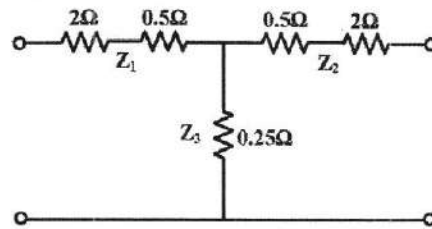
12. The impedance parameters Z_{11} and Z_{12} of the two-port network in the figure are

- $Z_{11} = 2.75 \Omega$ and $Z_{12} = 0.25 \Omega$
- $Z_{11} = 3 \Omega$ and $Z_{12} = 0.5 \Omega$
- $Z_{11} = 3 \Omega$ and $Z_{12} = 0.25 \Omega$
- $Z_{11} = 2.25 \Omega$ and $Z_{12} = 0.5 \Omega$



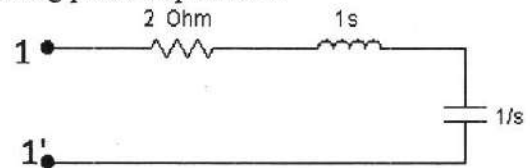13. For the network shown in the figure, find the driving point impedance.

- $(s^2 - 2s + 1)/s$
- $(s^2 + 2s + 1)/s$
- $(s^2 - 2s - 1)/s$
- $(s^2 + 2s - 1)/s$



14. Transfer admittance function is the ratio of Laplace transforms of _____

- Current at one port to voltage at other port
- Voltage at one port to current at other port
- Current at one port to current at other port
- Voltage at one point to voltage at other port

15. Find the Laplace transform of ramp function $r(t) = t$.

- $1/s$
- $1/s^2$
- $1/s^3$
- $1/s^4$

16. The integration of a square wave will result in

- Impulse function
- Ramp function
- Triangular wave
- Sinusoidal wave

17. The hybrid parameters of a two-port network h_{11} , h_{12} , h_{21} and h_{22} are respectively called
- Short-circuit input impedance, short-circuit current gain, open-circuit reverse voltage gain and open-circuit output admittance
 - Short-circuit input impedance, open-circuit output admittance, short-circuit current gain and open-circuit reverse voltage gain
 - Open-circuit reverse voltage gain, open-circuit output admittance, short-circuit input impedance and short-circuit current gain
 - Open-circuit reverse voltage gain, short-circuit current gain, open-circuit output admittance and short-circuit input impedance
18. The system is said to be stable if
- Gain margin is positive, phase margin is positive
 - Gain margin is positive, phase margin is negative
 - Gain margin is negative, phase margin is positive
 - Gain margin is negative, phase margin is negative
19. Bode plot of a network function consists of
- Magnitude vs phase plot, frequency vs phase plot
 - Magnitude vs frequency plot, frequency vs phase plot
 - Magnitude vs frequency plot, phase vs frequency plot
 - Magnitude vs phase plot only
20. The magnitude plot of $G(s) = s^2$ will have a straight line with slope of
- +20 db/decade
 - 20 db/decade
 - +40 db/decade
 - 40 db/decade

KATHMANDU UNIVERSITY
End Semester Examination [C]
December, 2024

Level : B.E.
Year : II
Time : 2 hrs. 30mins.

19 DEC 2024

Course : EEG 213
Semester : I
F. M. : 40


SECTION "B"

[4Q. × 10 = 40 marks]

Attempt ANY FOUR questions.


1.

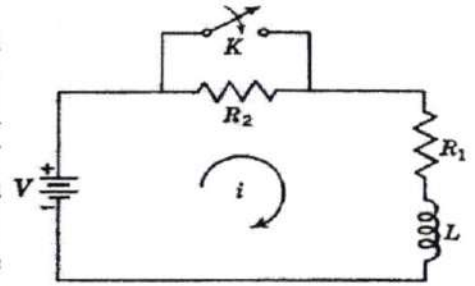- a. What is a time constant? Explain briefly with an example. [2]
- b. In the circuit shown in the figure below, the switch K is closed at $t = 0$, a steady-state having previously been attained. Solve for the current in the circuit as a function of time. [6]
- c. Briefly explain the physical interpretation of the response of the circuit. [2]




2.

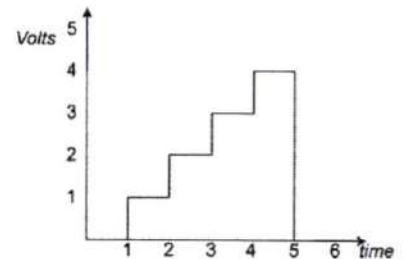- a. What are natural response and forced response? [2]
- b. Describe different types (or cases) of transient responses of a simple series or parallel RLC circuits. [5]
- c. Write an equation for the staircase waveform shown in the figure below in terms of unit step functions. [3]



3.

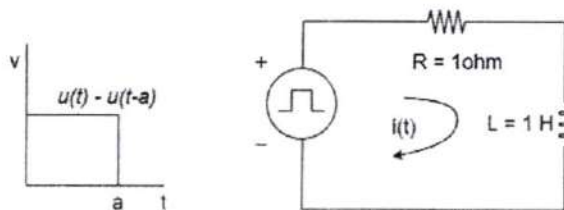- a. At $t = 0$, a pulse of width a as shown in the figure below (left) is applied to the RL network shown in the figure below (right). Determine the expression for the current $i(t)$ by using Laplace transform method.



- b. How are a ramp and an impulse function related to a step function? Define unit step, unit ramp and unit impulse function with a suitable figure


P.T.O.

4.

- a. Expand the following functions as partial fractions: [4]

$$M(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$$

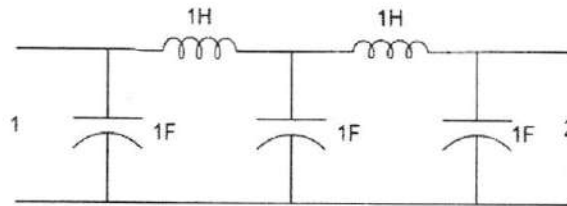
- b. Determine the transfer function $G_{12}(s)$ of the given network. [4]



- c. What are poles and zeros of a network? Explain with example. [2]

5.

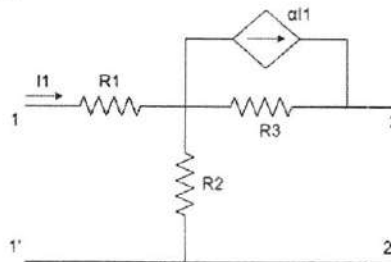- a. The network on the given figure represents a certain transistor. For this network, determine h parameters [4]



- b. For the network shown in the figure below, determine the y -parameters. [6]

